



Course Name: Digital System Design

Course Number and Section: 14:332:437:02

Experiment: Lab 7

Lab Instructor: Zhenghao Li

Date Performed: 10/29/24

Date Submitted: 11/12/24

Submitted by: Nikhil Chandra Donepudi Venkata Sambasiva

Prelab

Data Memory

```
1  module data_memory(  
2      input logic clk, rst,  
3      input logic [31:0] A,    //address  
4      input logic [31:0] WD,   //input data  
5      input logic WE,         // write enable  
6      output logic [31:0] RD,  
7      output logic [31:0] prode // check data in data_memory  
8  );  
9  
10     logic [31:0] mem_array [255:0];  
11     assign RD = mem_array[A[7:0]];  
12     assign prode = RD; |  
13  
14     always_ff @(posedge clk or negedge rst)  
15     begin  
16         if (!rst) begin  
17             for (int i = 0; i < 256; i++) begin  
18                 mem_array[i] <= i;  
19             end  
20         end  
21         else begin  
22             if (WE) begin  
23                 mem_array[A[7:0]] <= WD;  
24             end  
25         end  
26     end  
27 endmodule  
28
```

MUX_ALUSrc

```
1  module MUX_ALUSrc(  
2      input logic ALUSrc,           //select signal  
3      input logic [31:0] fromReg,   //from regfile  
4      input logic [31:0] fromImm,   //immediate value  
5      output logic [31:0] ALUSrc_out //output data  
6  );  
7      |  
8      assign ALUSrc_out = ALUSrc ? fromReg : fromImm;  
9  
10 endmodule
```

MUX_RegDst

```
1 module MUX_RegDst(  
2     input logic [4:0] RT,           // rt field of instruction  
3     input logic [4:0] RD,           // rd field of instruction  
4     input logic RegDes,             // Select signal  
5     output logic [4:0] RegDes_out   // Output data  
6 );  
7  
8     assign RegDes_out = RegDes ? RT : RD;  
9  
10 endmodule  
11
```

MUX_MemtoReg

```
1 module MUX_MemtoReg(  
2     input logic MemtoReg,  
3     input logic [31:0] ALUResult,  
4     input logic [31:0] RD, //from data memory  
5     output logic [31:0] MemtoReg_out  
6 );  
7  
8     assign MemtoReg_out = MemtoReg ? RD : ALUResult;  
9  
10 endmodule
```

SignExtend

```
1 module SignExtend(  
2     input logic [15:0] imm,  
3     output logic [31:0] signImm  
4 );  
5     assign signImm = {{16{imm[15]}}, imm}; // Sign extends  
6 endmodule  
7
```

Top

```

1  module top(
2      input logic clk, rst,
3      input logic[1:0] sw, //address for instruction memory
4      output logic[31:0] ALUResult, //output for pre-lab simulation
5      output logic[31:0] RD1, RD2, //output for pre-lab simulation
6      output logic[31:0] probe_register_file, //output for pre-lab simulation
7      output logic[6:0] display_led //output for in-lab
8  );
9
10 logic[31:0] inst_0 = 32'b0;
11 logic[31:0] inst_1 = 32'b010101_00000_00001_0000_0000_0000_0101; // LW instruction
12 logic[31:0] inst_2 = 32'b010100_00000_00110_0000_0000_0000_0010; // SW instruction
13 logic[31:0] inst_ex;
14 assign inst_ex = (sw==1)? inst_1:(sw==2)? inst_2: inst_0;
15
16 // Intermediate signals for connections
17 logic [4:0] regDst_out;
18 logic [31:0] signImm, memData, ALU_in2, MemtoReg_out;
19 logic MemtoReg, ALUSrc, WE;
20
21 assign ALUSrc = 1;
22 assign RegDst = 0;
23 assign MemtoReg = (inst_ex[31:26] == 6'b010101);
24 assign WE3 = (inst_ex[31:26] == 6'b010101);
25 assign WE = (inst_ex[31:26] == 6'b010100); // store
26 assign ALUControl = 3'b010; // sample control signal for ALU
27
28 module register_file r_f(
29     .clk(clk),
30     .rst(rst),
31     .A1(inst_ex[25:21]), // rs
32     .A2(inst_ex[20:16]), // rt
33     .A3(regDst_out), // rd or rt based on RegDst
34     .WD3(MemtoReg_out), // Data to write back to register file
35     .WE3(WE),
36     .RD1(RD1),
37     .RD2(RD2),
38     .probe(probe_register_file)
39 );
40

```

```

41 // Data Memory Instantiation
42 data_memory dm(
43     .clk(clk),
44     .rst(rst),
45     .A(ALUResult),
46     .WD(RD2),
47     .WE(WE),
48     .RD(memData),
49     .prode()
50 );
51
52 ALU t1(
53     .SrcA(RD1),
54     .SrcB(ALU_in2),
55     .ALUControl(inst_ex[29:27]),
56     .ALUResult(ALUResult)
57 );
58
59 // MUX for MemtoReg
60 MUX_MemtoReg mux_memtoreg(
61     .MemtoReg(inst_ex[31]),
62     .ALUResult(ALUResult),
63     .RD(memData),
64     .MemtoReg_out(MemtoReg_out)
65 );
66
67 // MUX for ALUSrc
68 MUX_ALUSrc mux_alusrc(
69     .fromReg(RD2),
70     .fromImm(signImm),
71     .ALUSrc(inst_ex[28]),
72     .ALUSrc_out(ALU_in2)
73 );
74
75 // MUX for RegDst
76 MUX_RegDst mux_regdst(
77     .RT(inst_ex[20:16]),
78     .RD(inst_ex[15:11]),
79     .RegDes(inst_ex[26]),
80     .RegDes_out(regDst_out)
81 );
82


```

```


83 // Sign Extend Module
84 SignExtend sign_ext(
85     .imm(inst_ex[15:0]),
86     .signImm(signImm)
87 );
88
89 display t2(
90     .data_in(ALUResult),
91     .segments(display_led)
92 );
93
94 endmodule

```

Waveform

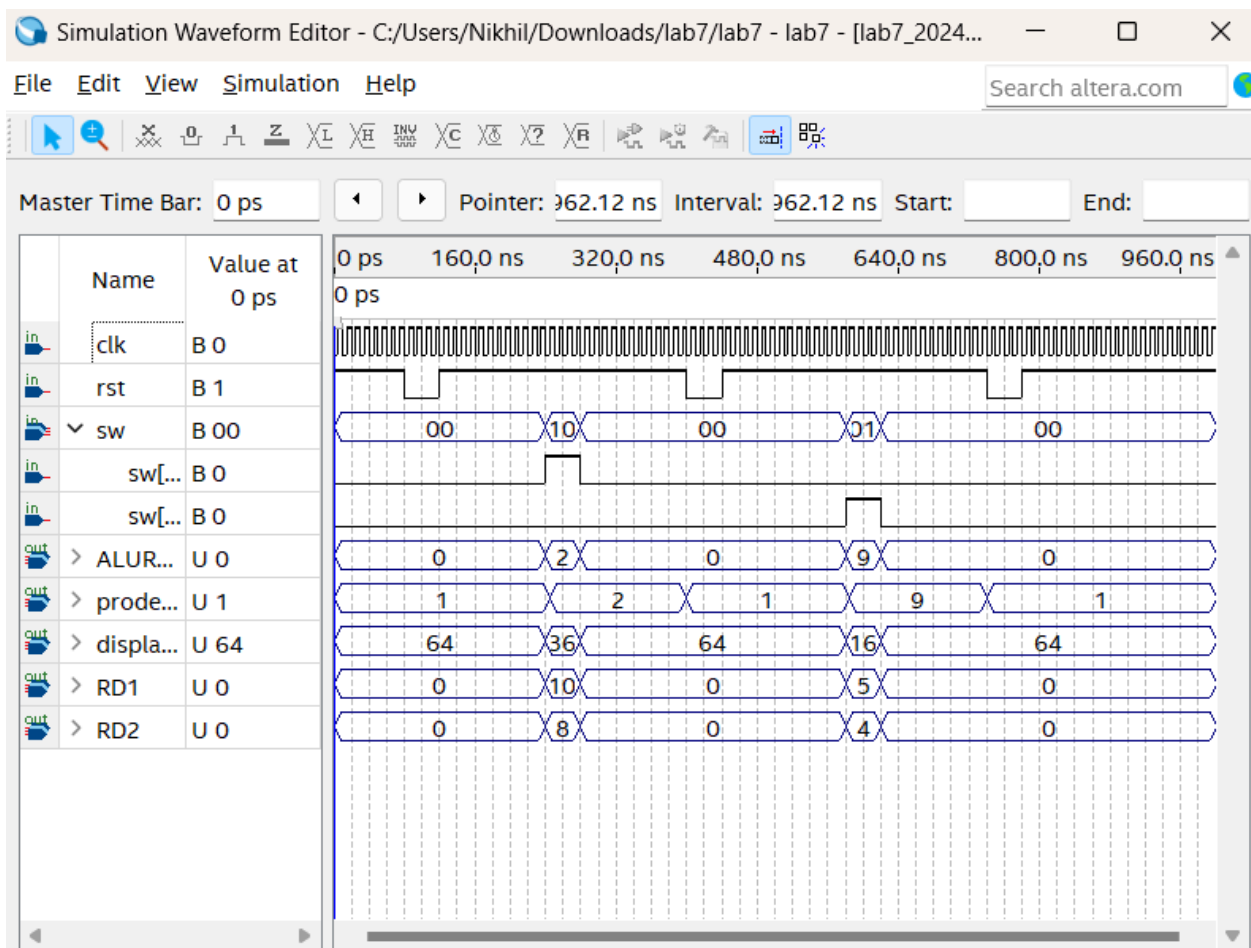


PreLab values

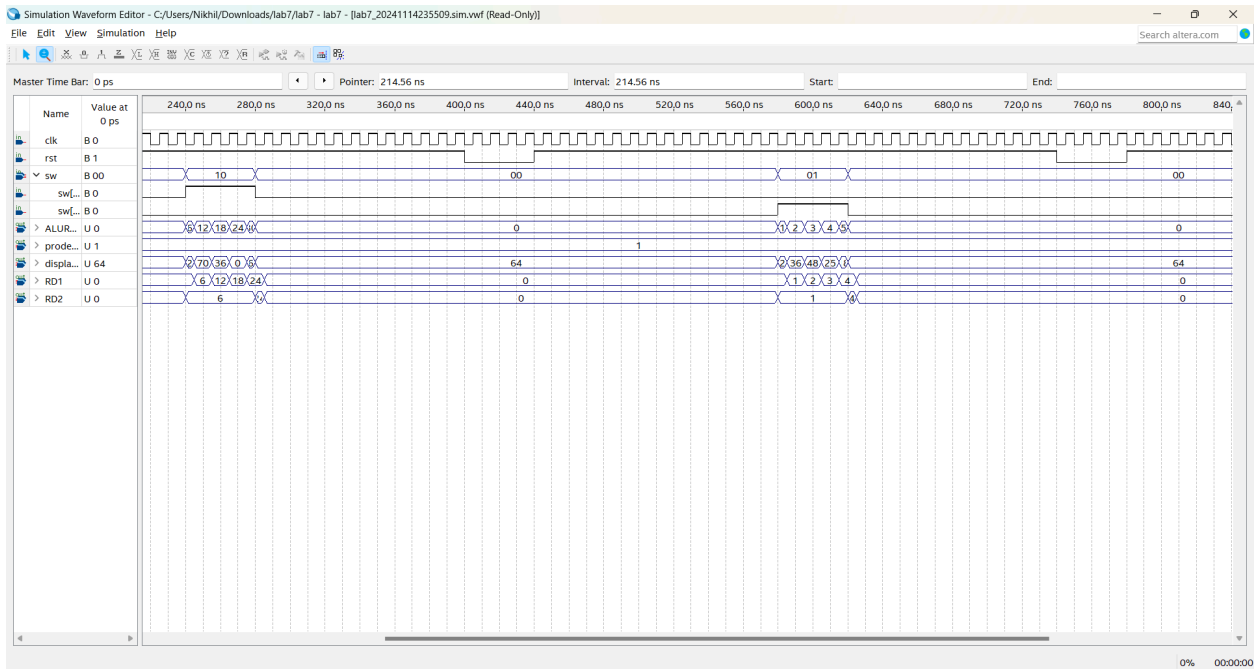


Board number: 514


SW - register file[4] to data memory[2]

 

LW - register_file[5] → data_memory[1]

 

Pin assignment:

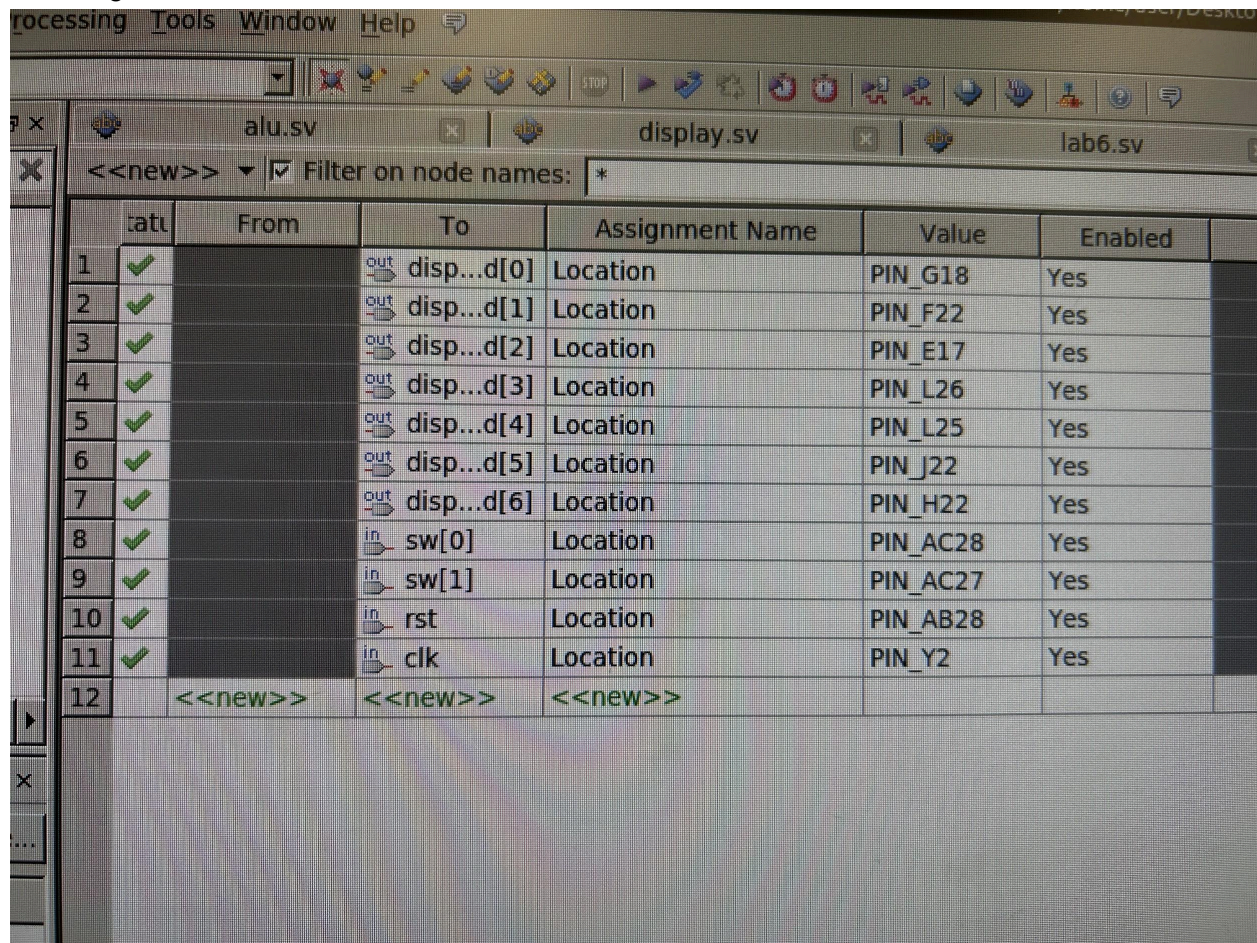

		From	To	Assignment Name	Value	Enabled
1	✓		out disp...d[0]	Location	PIN_G18	Yes
2	✓		out disp...d[1]	Location	PIN_F22	Yes
3	✓		out disp...d[2]	Location	PIN_E17	Yes
4	✓		out disp...d[3]	Location	PIN_L26	Yes
5	✓		out disp...d[4]	Location	PIN_L25	Yes
6	✓		out disp...d[5]	Location	PIN_J22	Yes
7	✓		out disp...d[6]	Location	PIN_H22	Yes
8	✓		in sw[0]	Location	PIN_AC28	Yes
9	✓		in sw[1]	Location	PIN_AC27	Yes
10	✓		in rst	Location	PIN_AB28	Yes
11	✓		in clk	Location	PIN_Y2	Yes
12		<<new>>	<<new>>	<<new>>		